

## Medical Electronics – Laboratory 2

### Exercise 1

Build a circuit that displays number 10 on the 2-digit 7-segment display.

Schematic of a 1-digit 7-segment display:

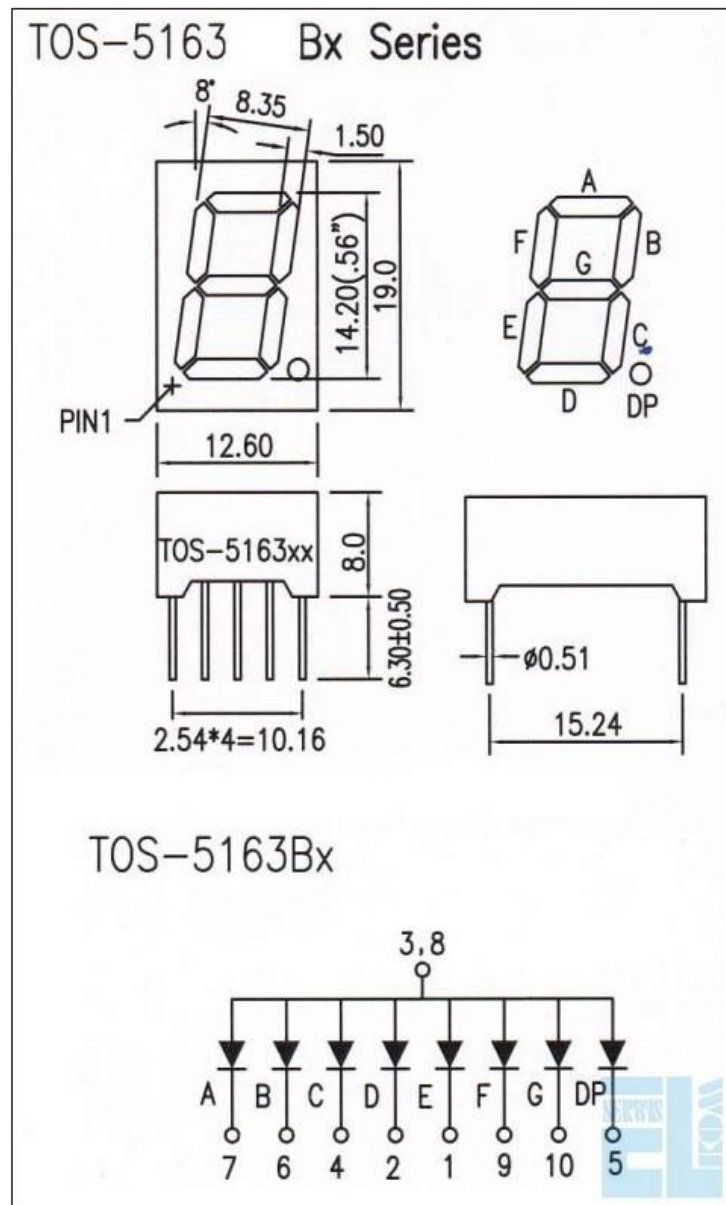


Figure 1 Documentation for the 7-segment display

Pins are counted in the anti-clockwise direction, starting from pin 1 at the left bottom corner.

Ports D4 and D5 on Arduino board are the control ports for digit 1 and 2. Segments of the digit from A to G are connected to Arduino ports D6-D12. Place the displays on the breadboard next to each other so that each pin is placed in the separate column. Use other 9 columns for connection to the Arduino board. The connection is presented in Figure 2. The relation between segments A(a)-G(g) is given in Figure 1. Complete circuit is shown in Figure 3.

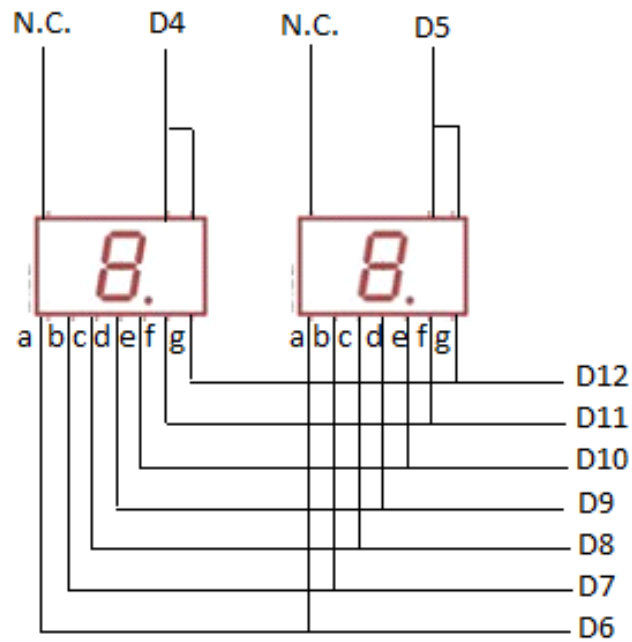


Figure 2 Connection of 2 7-segment displays to Arduino board

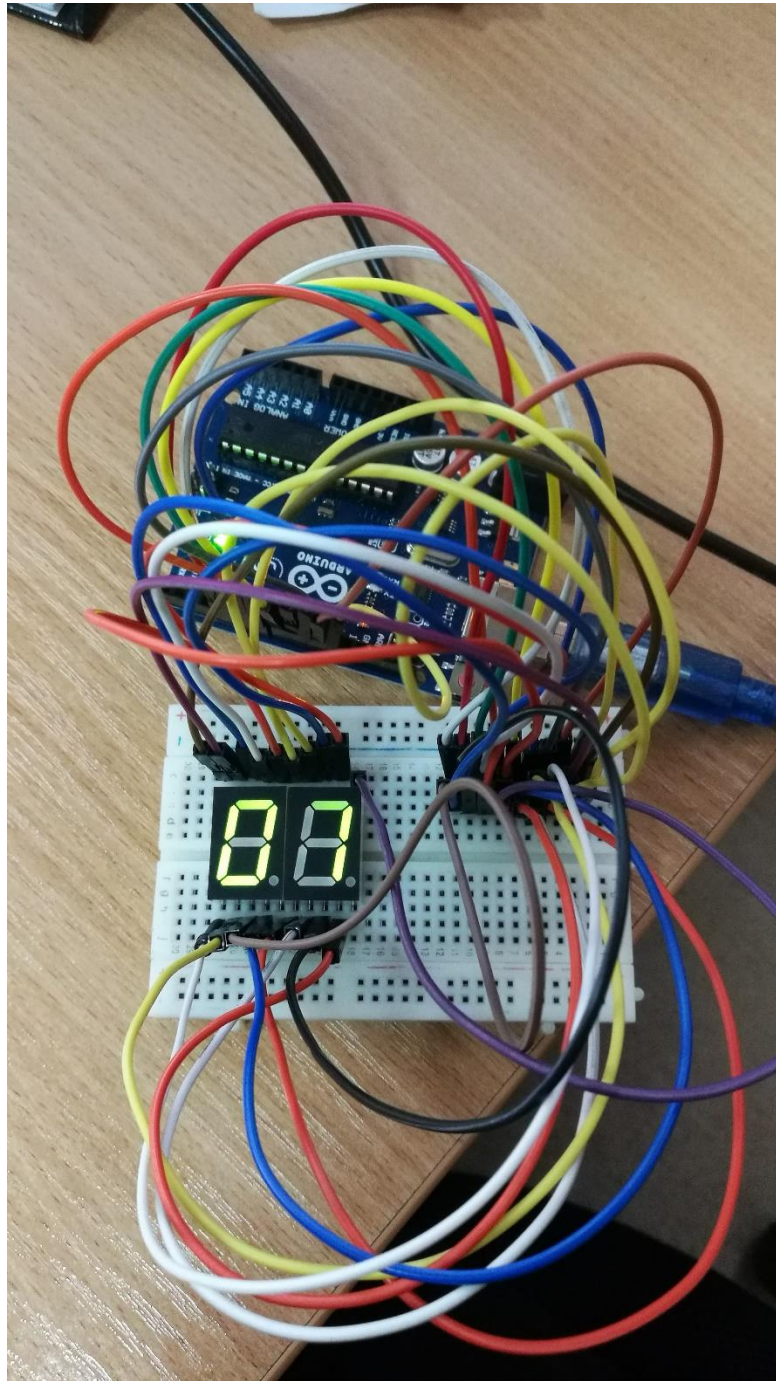


Figure 3 Complete circuit

The code for displaying number 10 is as follows:

```
#include "SevSeg.h"

SevSeg sevseg;

int a = 10;

unsigned long timer;

void setup() {
    sevseg.Begin(1,2,3,4,5,6,7,8,9,10,11,12,13);
}

void loop() {
    // put your main code here, to run repeatedly:
    sevseg.PrintOutput();
    unsigned long mils=millis();
    if (mils-timer>=1000)
    {
        timer=mils;
        sevseg.NewNum(a, (byte) 2);
    }
}
```


## **Exercise 2**

Modify the code for the 2-digit 7-segment display to count from 0 to 10 in a loop in 1 second intervals.

## **Exercise 3**

The LM35 series are precision integrated-circuit temperature devices with an output voltage linearly proportional to the Centigrade temperature. The LM35 device does not require any external calibration or trimming to provide typical accuracies of  $\pm\frac{1}{4}^{\circ}\text{C}$  at room temperature and  $\pm\frac{3}{4}^{\circ}\text{C}$  over a full  $-55^{\circ}\text{C}$  to  $150^{\circ}\text{C}$  temperature range. Schematic of output pins in LM35 is presented in Figure 4.

# TO-92 Plastic Package

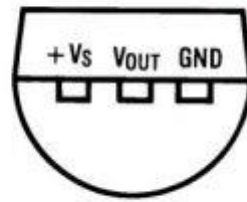

**BOTTOM VIEW**  
DS005516-2

Figure 4 LM35 output pins

Build a circuit with LM35 temperature sensor (Figure 5).

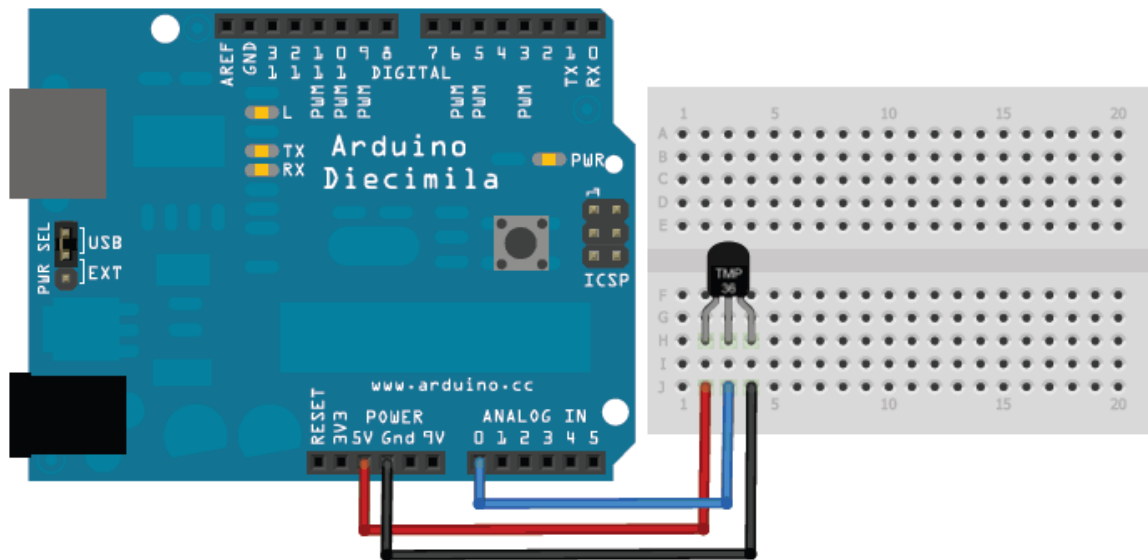


Figure 5 Connection for LM35 sensor

Implement a code to display the readings from LM35 sensor in the serial monitor of Arduino IDE:

```
int refreshTime = 500; //how many seconds should it wait before it
//checks and displays the temp again? 1000 = 1 second

unsigned long timer;

float temperature = 0;

void setup() {
    Serial.begin(9600);
}

void loop() {
    //Reads the input and converts it to Celsius degrees
    temperature = analogRead(0) * 0.004882812 * 100;

    unsigned long mils=millis();
    if (mils-timer>=refreshTime) {
        timer=mils;
        //Print teperature in serial monitor
        Serial.println(temperature);
    }
}
```

Observe the output in Serial Monitor (Figure 6) and the plot (Figure 7) when keeping the sensor in your fingers to increase the temperature.

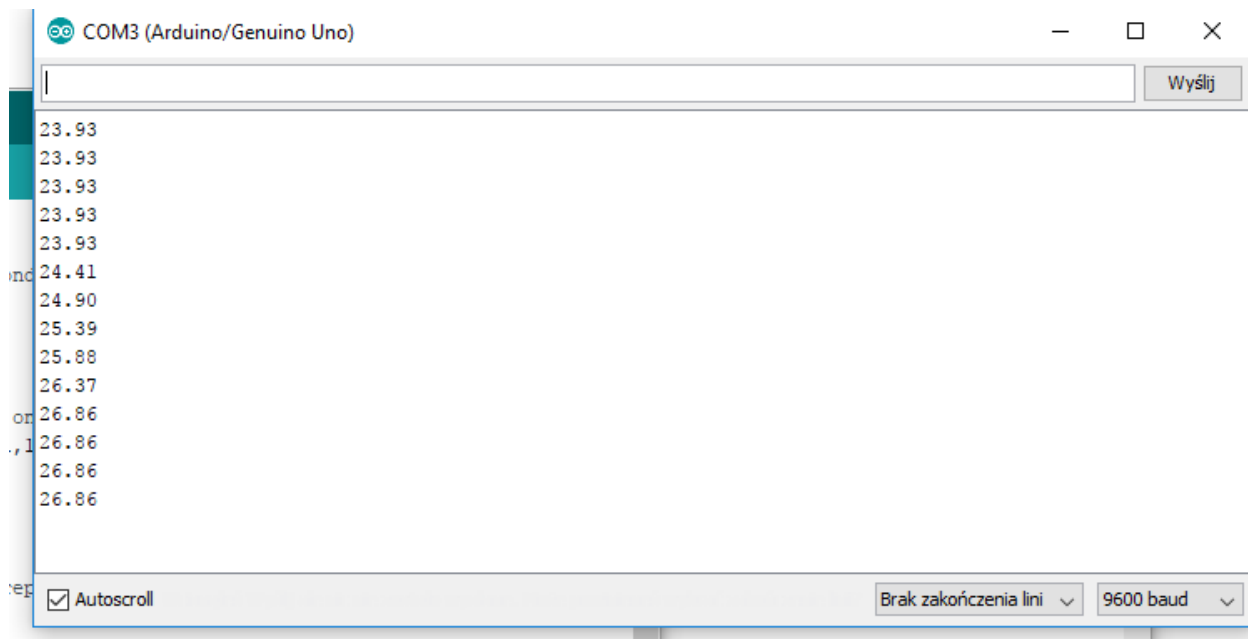


Figure 6 Data displayed in serial monitor

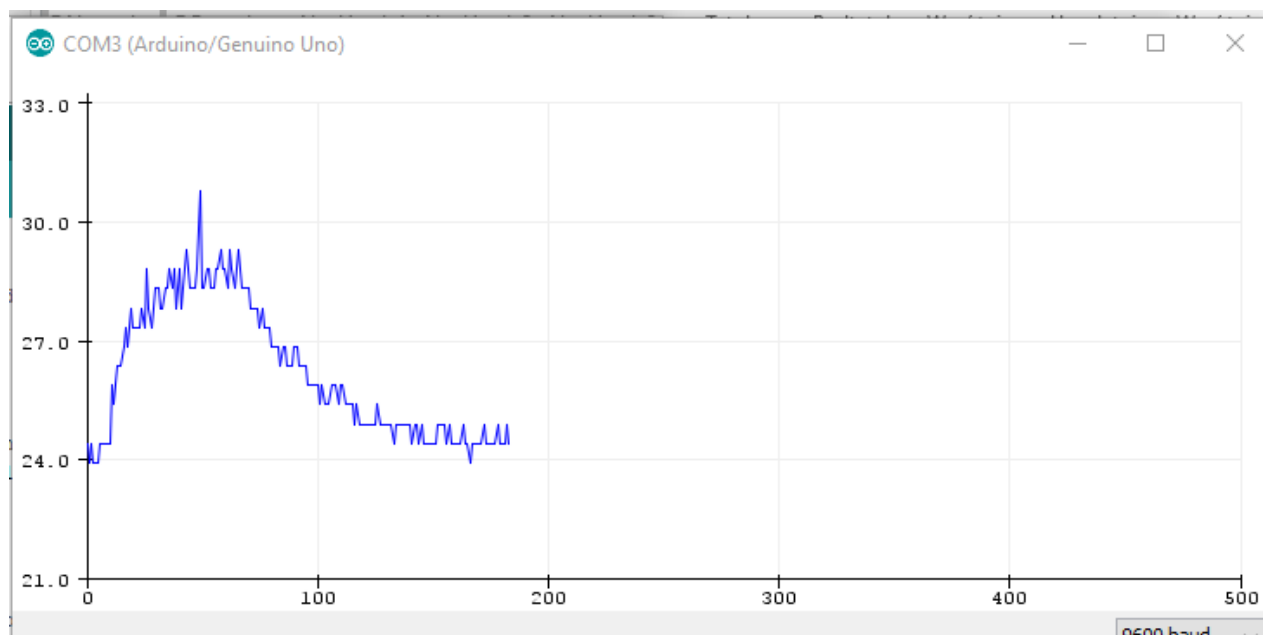


Figure 7 Plotted data from temperature LM35 sensor

## Exercise 4

Modify the code using the code from Exercise 1 to display the temperature from the sensor using 7-segment display.